



# Fundamental Algorithms for System Modeling, Analysis, and Optimization

Edward A. Lee, Jaideep Roychowdhury,  
Sanjit A. Seshia

UC Berkeley

EECS 244

Fall 2016

Lecturer: Yu-Yun Dai

Copyright © 2010-date, E. A. Lee, J. Roychowdhury,  
S. A. Seshia, All rights reserved

**Timing Analysis**


Thanks to Kurt Keutzer for several slides

# Why Does Timing Analysis Matter?


- (Clock) Speed is one of the major performance metrics for digital circuits

Timing Analysis = the process of verifying that a chip meets its speed requirement

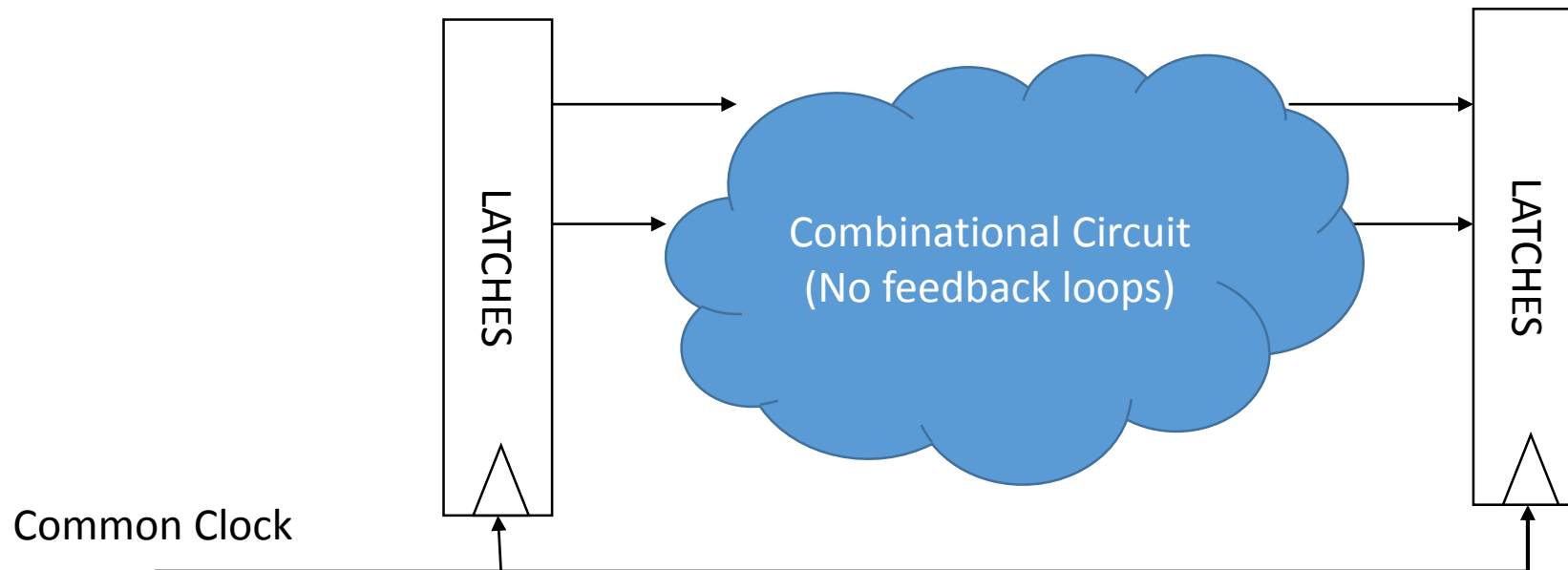- Determine fastest permissible clock speed (e.g. 1 GHz) by determining delay of longest path from register to register (e.g. 1ns.)




# Path Space in Program

 

```
void altitude_control_task(void) {  
→ if (pprz_mode == PPRZ_MODE_AUTO2  
    || pprz_mode == PPRZ_MODE_HOME) {  
→ if (vertical_mode == VERTICAL_MODE_AUTO_ALT) {  
    /* inlined below: function altitude_pid_run(); */  
    float err = estimator_z - desired_altitude;  
    desired_climb = pre_climb + altitude_pgain * err;  
    if (desired_climb < -CLIMB_MAX)  
        desired_climb = -CLIMB_MAX;  
→ if (desired_climb > CLIMB_MAX)  
        desired_climb = CLIMB_MAX;  
    }  
    }  
}
```

Must find:  
Longest path in the control-flow  
graph (CFG)

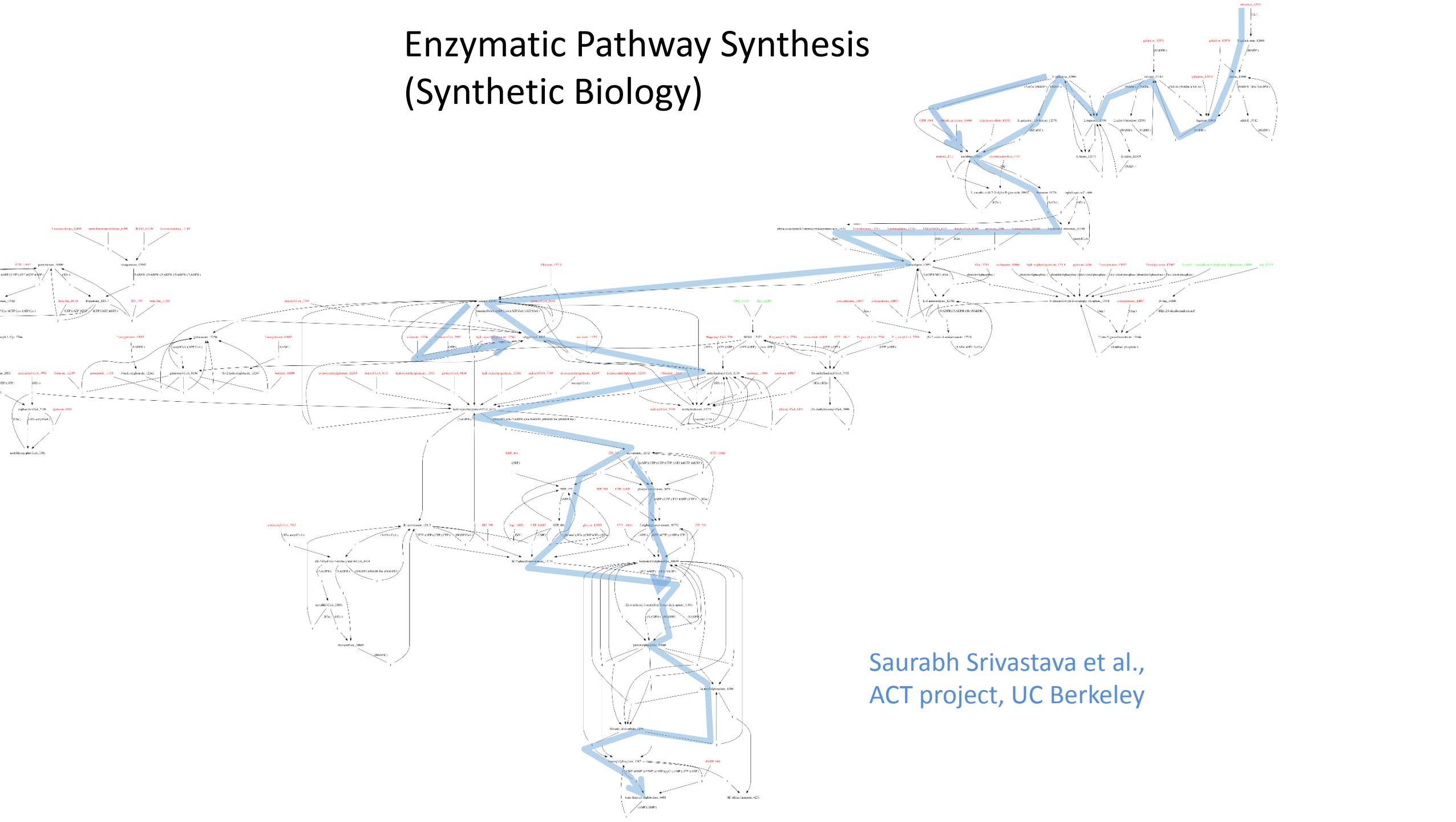
# Enzymatic Pathway Synthesis (Synthetic Biology)



Saurabh Srivastava et al.,  
ACT project, UC Berkeley

 
# Timing Analysis for Circuits

- Consider a signal in a clocked design:
  - The value varies between one (high-voltage) and zero (low-voltage)
  - Changes can occur at different times in each cycle
    - Time required for change depends on input patterns
    - May not change at all in some cycles
    - May make multiple changes before settling to a final value


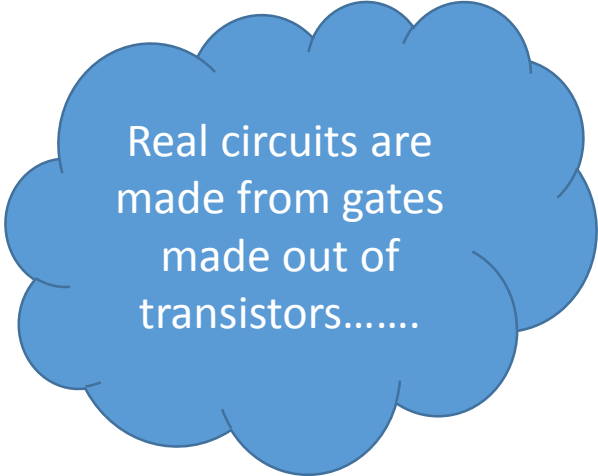
# Static Timing Analysis


- “Static” means we are not doing simulation (dynamic)
- Consider the worst case
  - Assume that signal becomes *stable* at latest possible time
  - Assume signal becomes *unstable* at the earliest possible time




Real circuits are  
made from gates  
made out of  
transistors.....
 
# Timing Analysis: Basic Model


- Set up/Cycle time: Does data always **reach** a stable value at all latch inputs in time for the clock to capture it?
  - Look at **late mode** timing, or **longest path**
- Hold time: Does data always **stay** stable at all latch inputs long enough after the clock to get stored?
  - Determine this by looking at **early mode** timing, or **shortest path**



$$T_{\text{max}} \leq T$$

 

 
$$T_{\text{max}} + T_{\text{setup}} \leq T$$



$$T_{\text{min}} \geq T_{\text{hold}} + T_{\text{skew}}$$
 
# Timing Analysis: Topological and Functional

- Do we worry about “gate function”?
  - Logical timing analysis: **YES**, We care “false path”
  - Topological timing analysis: **NO**, we only worry about the delay through the paths => overestimate






# We will Learn


- False path v.s. True path
  - Static Sensitization
  - Static Co-sensitization
- Algorithms to find the longest path in a DAG
  - Incremental longest path in a DAG
  - Top k longest paths in a DAG
- Sequential synthesis: Retiming\*
 
# False Paths (consider Transition Mode)

A path is false if it cannot be responsible for the delay of a circuit




**Length of  
sensitized path = 5**

 


Graph model implies path of length 6
 
# False Paths

A path is false if it cannot be responsible for the delay of a circuit



Length of  
sensitized path = 5

 


Graph model implies path of length 6


# False vs. True Paths

- TRUE path = one that can be responsible for the delay of a circuit
- Need techniques to find whether a path is TRUE or FALSE

 
# The Fixed Delay Model: Constant Delay for Each Gate (or Wire)



 
**Transition delay is 0, for both input transitions.  
Consider the “faster” circuit**


 
# Paradoxical Behavior with the Transition Model?



 **Transition delay is 0, for both input transitions.  
Consider the “faster” circuit**




# Problems with Fixed Delay + Transition Model

1. Transition model can be tricky to reason about
  2. Fixed gate delays are unrealistic, due to manufacturing process variations
- More realistic delay model: *Lower and upper bounds*
  - Perform timing analysis for a whole family of circuits that share the same lower/upper bounds
 
# Fixed Delays $\rightarrow$ Bounded Delays

Want algorithms that report the **critical path delay** of the **slowest circuit** in the circuit family



Delay of 6 for the above circuit for transition model  
(longest path that can propagate a transition)



# Floating-Mode Delay Model

Input transition  $\rightarrow$  Single input vector condition

Pessimistic, but easier to compute



# Floating-Mode Delay Model

Assume an input pair  $\langle v_1, v_2 \rangle$  has been applied, but we only look at  $v_2$  -- i.e. node values are unknown until set by  $v_2$   
(pessimistic because we assume any  $v_1$  can be adversarially selected, to reason about long paths)



Assume the 1 at the input of the AND arrives before the 0 (even if in reality it arrives later and the gate output stays at 0 throughout, and no path is sensitized).

# Roadmap for rest of lecture


- Consider conditions under which paths are TRUE or FALSE under the *floating-mode delay model with fixed delays*
- + under floating-mode model, fixed and bounded delays yield same worst-case circuit delay (for same upper bounds)
- + worst-case delay under floating-mode model is upper bound on that under the transition model

# Controlling and Non-Controlling Values

- A **controlling value** at a gate input is the value that determines the output value of that gate irrespective of the other input value.
- (the output value is called a **controlled value**)
- A **controlling** value for an AND gate is 0 and for an OR gate is 1. (The controlled values are 0 and 1 resp.)
- A **non-controlling** value for an AND gate is 1 and for an OR gate is 0.
- What about NAND and NOR gates?
 
# Static Sensitization

Definition: A path is statically sensitized by a vector  $V$ , if along each gate on the path, *if* the gate output is a controlled value, the input corresponding to the path is the *only* input with a controlling value




Input vector 100X statically sensitizes red path

# Static Sensitization


Static sensitization is **sufficient** for a path to be responsible for the delay of a circuit

WHY?

 


Input vector 100X statically sensitizes red path

# Is this path statically sensitizable?

 

Definition: A path is statically sensitized by a vector  $V$ , if along each gate on the path, if the gate output is a controlling value, the input corresponding to the path is the only input with a controlling value

Is this path statically sensitizable?

 


No, red path is NOT statically sensitizable (work this out)



 
# More on Static Sensitization

Are paths a,d,f,g and b,d,f,g statically sensitizable?  
Are they true paths?


 
# Static Sensitization is too strong

A true path (one that is responsible for delay of a circuit) need not be statically sensitizable



Paths **a,d,f,g** and **b,d,f,g** are NOT statically sensitizable.  
But they are TRUE paths.

# Static Co-sensitization


Definition: A path is statically co-sensitized by a vector  $V$ , if the input corresponding to the path presents **a controlling value** at each gate along the path whose output is a controlled value.

Not necessarily the **ONLY** controlling value
 
# Static Co-sensitization

Definition: A path is statically co-sensitized by a vector  $V$ , if the input corresponding to the path presents a controlling value at each gate along the path whose output is a controlling value.

Not necessarily the **ONLY** controlling value




Paths a,d,f,g and b,d,f,g are statically co-sensitizable

# Static Co-sensitization and Delay

Static co-sensitization is **necessary** for a path to be responsible for the delay of a circuit. (WHY?)


Is it sufficient?

 

# Static Co-sensitization and Delay

Static co-sensitization is **necessary** for a path to be responsible for the delay of a circuit

But NOT sufficient

 

Path of length 6 is statically co-sensitized  
Delay of circuit is 5 (as observed earlier)

# Summary

Static sensitization (SS) sufficient for true path, but not necessary

Static co-sensitization (SC) necessary for true path, but not sufficient


Determining whether a path is SS/SC can be formulated as a SAT problem

# Modeling Timing in a Combinational Circuit

- Arrival time in green

Interconnect  
delay in  
red

Gate delay in  
blue


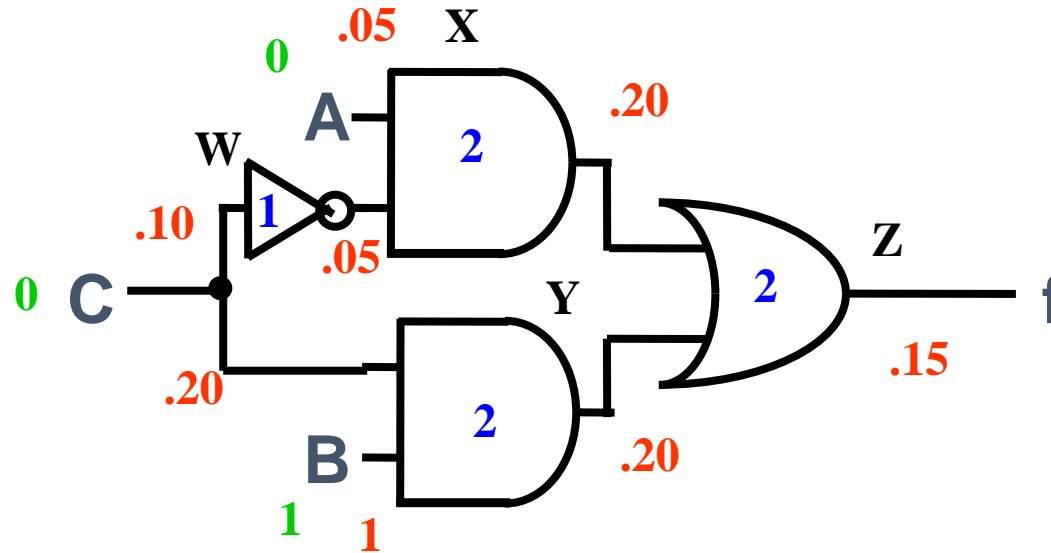


What's the right mathematical object to use to represent this physical object?


 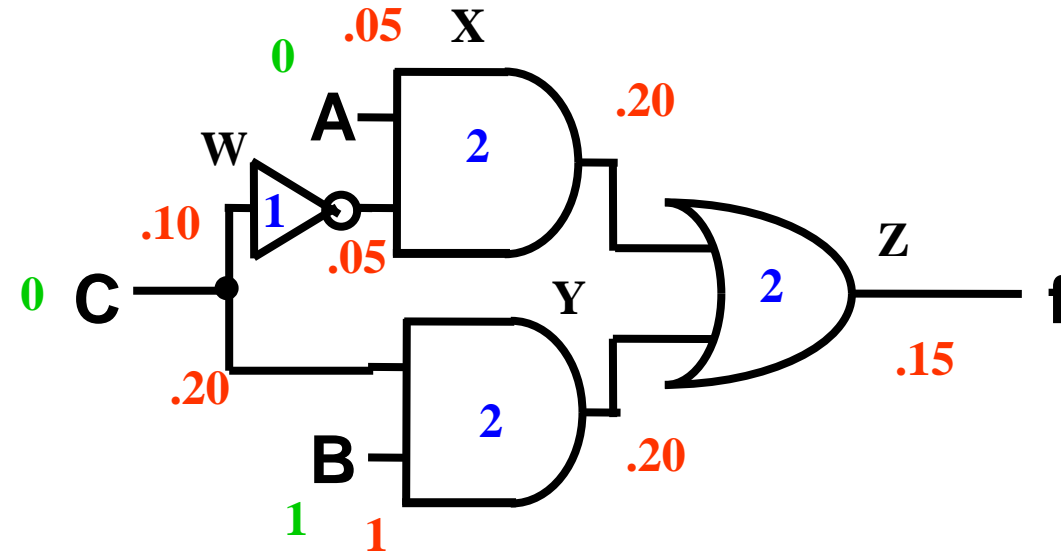
# Modeling - 1

- Use a labeled *directed graph*
- $G = \langle V, E \rangle$
- *Vertices* represent gates, primary inputs and primary outputs
- *Edges* represent wires
- *Labels* represent delays
- Now what do we do with this?




# Modeling - 2


- Find longest path in a directed graph  $G = \langle V, E \rangle$

- What sort of directed graph do we have?

 
- Is this in the standard form for a longest/shortest path problem?



# Split Nodes into Edges

 


# DAG with Weighted Edges

 

Problem: Find the longest (critical) path from source  $s$  to sink  $f$ .
 
# Naïve Approach: Enumerate Paths

How many paths in this example?  
In the worst case?



Problem:

Find the longest path from source **s** to sink **f**.

# Algorithm 1: Longest path in a DAG

Critical Path Method [Kirkpatrick 1966, IBM JRD]

Let  $w(u,v)$  denote weight of edge from  $u$  to  $v$

Steps:

1. Topologically sort vertices

order:  $v_1, v_2, \dots, v_n$       $v_1 = s, v_n = ?$

2. For each vertex  $v$ , compute

$d(v)$  = length of longest path from source  $s$  to  $v$

$d(v_1) = 0$

For  $i = 2..n$

$d(v_i) = \max_{\text{all incoming edges } (u, v_i)} d(u) + w(u, v_i)$

# Algorithm 1: Longest path in a DAG

Critical Path Method [Kirkpatrick 1966, IBM JRD]

Let  $w(u,v)$  denote weight of edge from  $u$  to  $v$

Steps:

1. Topologically sort vertices

order:  $v_1, v_2, \dots, v_n$       $v_1 = s, v_n = f$

Time Complexity?

$O(m+n)$

2. For each vertex  $v$ , compute

$d(v)$  = length of longest path from source  $s$  to  $v$

$d(v_1) = 0$


For  $i = 2..n$

$d(v_i) = \max_{\text{all incoming edges } (u, v_i)} d(u) + w(u, v_i)$

Run the CPM on our example
 
# Algorithm 2: Incremental longest path in a DAG

Suppose only a few weights/nodes/edges change.  
How do we recompute the longest path efficiently?



Exercise: READ HANDOUT



# Algorithm 3: Top k longest paths in a DAG

Often, we don't want just the longest path

Want to find the *top k longest paths*

How to do this efficiently? (i.e., polynomial in  $n$ ,  $m$ ,  $k$ )

Key insight/idea:

- The 2nd longest path shares a prefix with the longest path.
- From each node along longest path, keep track of the “next longest” route to sink  $f$ .

# Algorithm 3: Top k longest paths in a DAG

Pre-compute phase:

1.  $\delta(v)$  = length of longest path from vertex  $v$  to sink  $f$ .

How to compute? Complexity?

2. At each vertex  $v$ : order successor vertices  $u_1, u_2, \dots, u_k$  by decreasing  $\text{cost}(u_i) = w(v, u_i) + \delta(u_i)$
3. Compute 'branch' slacks at  $v$ :  $\text{bs}_i(v) = \text{cost}(u_i) - \text{cost}(u_{i+1})$   
 $\text{bs}_k(v) = \text{cost}(u_k)$

# Algorithm 3: Top k longest paths in a DAG


## Pre-compute phase:

1.  $\delta(v)$  = length of longest path from vertex  $v$  to sink  $f$ .  
How to compute? Complexity?
2. At each vertex  $v$ : order successor vertices  $u_1, u_2, \dots, u_k$  by decreasing  $\text{cost}(u_i) = w(v, u_i) + \delta(u_i)$
3. Compute 'branch' slacks at  $v$ :  $\text{bs}_i(v) = \text{cost}(u_i) - \text{cost}(u_{i+1})$   
 $\text{bs}_k(v) = \text{cost}(u_k)$


## Main phase:

1. Let longest path  $p = s, v_1, v_2, \dots, v_r, f$
2. For 2<sup>nd</sup> (next) longest, order nodes according to branch slacks:  $\text{bs}_1(s), \text{bs}_1(v_1), \dots, \text{bs}_1(v_r)$ , and pick the smallest. The corresponding successor indicates the next longest path.
3. For 3<sup>rd</sup> longest, add nodes along 2<sup>nd</sup> longest to the ordered node list, maintaining order. Go back to step 2 (check 'next' branch slack). (see handout for details)

# Example: Top k longest paths in a DAG

 

# Example: Top k longest paths in a DAG

 

# Bibliography

- S. Devadas, K. Keutzer, S. Malik: “Computation of Floating Mode Delay in Combinational Circuits: Theory and Algorithms”, IEEE TCAD, December 1993.
- Sachin Sapatnekar , “Timing”, Chapter 5-”Timing Analysis for Combinational Circuits”, Springer-Verlag New York, Inc. 2004
- E. A. Lee and S. A. Seshia , Chapter 15 of “Introduction to Embedded Systems” , <http://leeseshia.org>