



Fundamental Algorithms for System Modeling, Analysis, and Optimization

Edward A. Lee, Jaideep Roychowdhury,
Sanjit A. Seshia

UC Berkeley
EECS 144/244
Fall 2011

Copyright © 2010-11, E. A. Lee, J. Roychowdhury,
S. A. Seshia, All rights reserved

Sequential Equivalence Checking

Thanks to Kurt Keutzer and Rob Rutenbar for several slides

Lecture Outline

What we know:

- How to check two combinational circuits for equivalence

What we need:

- Checking equivalence of sequential circuits
- E.g., a circuit and its retimed version

Today's lecture is about using Boolean function manipulation & BDDs for doing this

- Basics
- Sequential equivalence checking: the problem
- Algorithms

Two Operations on Cofactors

Given: $F(x_1, \dots, x_n)$

Define

$$C(x_2, \dots, x_n) = F_{x_1} \cdot F_{x_1'} \quad \leftarrow \text{“Consensus”}$$

$$S(x_2, \dots, x_n) = F_{x_1} + F_{x_1'} \quad \leftarrow \text{“Smoothing”}$$

What are the ON-sets of C and S in terms of the ON-sets of F_{x_1} and $F_{x_1'}$?

3

Example

$$F(a,b,c) = ab + bc + ac$$

$$F_a = b + c$$

$$F_{a'} = bc$$

$$C(b,c) = ?$$

$$S(b,c) = ?$$

4

Quantification

Consensus also called “universal quantification”

$$\begin{aligned} - C(x_2, \dots, x_n) &= F_{x_1} \cdot F_{x_1}' \\ &= \forall x_1 F(x_1, x_2, \dots, x_n) \text{ (“for all } x_1 \dots\text{”)} \end{aligned}$$

Smoothing also called “existential quantification”


$$\begin{aligned} - S(x_2, \dots, x_n) &= F_{x_1} + F_{x_1}' \\ &= \exists x_1 F(x_1, x_2, \dots, x_n) \text{ (“there exists } x_1 \dots\text{”)} \end{aligned}$$

5

Back to Equivalence Checking . . .


6

Equivalence Checking: Simple Case

 

7

Retimed circuits

 

Circuits are equivalent but it is not possible to show that they are equivalent using Boolean equivalence

8

Encoding Problems

Some circuit specifications are
“symbolic” rather than binary-valued

e.g. specification for an ALU

<u>Symbol</u>	<u>Operation</u>
ADD	+
SUB	-
XOR	Exclusive-OR
INC	Increment

Can assign any binary op code to the
symbolic values, so long as they are
different

9

Different State Encodings

Circuit 1

<u>Symbol</u>	<u>Operation</u>
ADD	00
SUB	01
XOR	10
INC	11


Circuit 2

<u>Symbol</u>	<u>Operation</u>
ADD	11
SUB	10
XOR	00
INC	01

Different state
encodings make
circuits no longer
amenable to
combinational
logic equivalence
checking

10

Different Encodings

 

11

A Fresh Look at Equivalence Checking

Given: Two sequential circuits, with same inputs and outputs

- But state bits might differ


Let's view this problem mathematically ("formally"):

A combinational circuit is a Boolean function.

A sequential circuit is a _____ ?

12

What's in a Finite-State Machine (FSM) ?

 

13

Finite-state machine (FSM) Equivalence

Equivalence checking problem:

Given: 2 FSMs, with same inputs/outputs


To check:

The output behavior of both machines is identical

- over all time points, starting from a common "initial" / "reset" state
- for every sequence of inputs

14

Visualizing the Problem: Compose FSMs

 

Q1. What goes inside the boxes?

Q2. How can we decide if the output is always 1?

15

What goes in the boxes

From the finite-state machine description, we write Boolean equations that describe


Next state as a function of present state & inputs

Output as a function of present state & inputs

Often this is how the system is most easily described

16

Example: FSM1

 

Denote next state encoding as p^+q^+ and output as z

$$p^+(x, p, q) = ?$$

$$pq' + p'x$$

$$q^+(x, p, q) = ?$$


$$p'x' + p'q$$

$$z(x, p, q) = ?$$

$$pq$$

17

 Example: FSM 2 (different state encoding)



Denote next state encoding as $a^+b^+c^+d^+$ and output as z

$$a^+(x, a, b, c, d) = ?$$

$$b^+(x, a, b, c, d) = ?$$

$$c^+(x, a, b, c, d) = ?$$


$$d^+(x, a, b, c, d) = ?$$

NOTE: We never start with a state graph like the one above – WHY?

$$z(x, a, b, c, d) = d$$

18

Back to the Problem

 

Q1. What goes inside the boxes? ✓

Q2. How can we decide if the output is always 1?

19

Rephrasing the Problem

Is the output always 1?

Can the output ever be 0?

Solved using “reachability analysis”

- Is there a state that the combined FSM can reach such that the output is 0?

20

Performing Reachability Analysis

3 Main ideas:

Represent sets as Boolean functions

- Use BDDs to represent Boolean functions

Represent FSMs “symbolically”

- FSM = set of states and set of transitions
- FSM can be encoded using BDDs

Perform Symbolic Reachability Analysis

- Start in initial state
- Compute set of states reachable from initial state in 1, 2, 3, ... clock ticks
- This computation must terminate – WHY?


21

1. Sets as Boolean functions

A Boolean function F of n variables x_1, x_2, \dots, x_n

$$F : \{0,1\}^n \rightarrow \{0,1\}$$

can be represented as set (its ON-set)

 

Similarly, for a set of size $\leq 2^n$, you can encode each element as a string of $\leq n$ bits

Each string can be viewed as a minterm

View the set as the ON-SET of a Boolean function

22

Set Operations as Boolean Operations

$A \cup B = ?$

$A \cap B = ?$

$A \subset B ?$

Is A empty?

23

2. Symbolic Encoding of FSM

FSM is

Set of states

- State encoding is a minterm
- This is what we want to compute!

Set of transitions

- To compute set of reachable states, we first need a way of encoding transitions

24

Encoding Transitions

Define a new function, δ , called the “transition function/relation”

δ (current state s , input x , next state s^+)


= 1 if we can go to s^+ from s on x

= 0 otherwise

i.e. δ encodes all legal transitions (“edges” in the state graph)

25

Example of δ

 

$$p^+ = pq' + p'x$$

$$q^+ = p'x' + p'q$$

$$z = pq$$

Just turn each Boolean eqn into Boolean identity (iff), and AND together the identities for each state bit

Denote next state encoding as p^+q^+ and output as z


$$\delta(p, q, x, p^+, q^+)$$

$$\delta(0, 0, 0, 0, 1) = ?$$

$$\delta(1, 1, 1, 1, 1) = ?$$

How to construct δ ?

- Pick an edge & encode it

 

- Add a term into the SOP for δ for that edge

$$\delta = p'q'x'p^+q^+ + \dots$$

- There's an easier way...

26

3. Reachability Analysis

Given:

A minterm corresponding to initial state R_0

δ

To find:

All states reachable from R_0 in 1, 2, 3, ... clock ticks

Idea:

Enumerate all states by repeatedly evaluating FSM equations, starting from an initial state?

27

3. Reachability Analysis

Given:

A minterm corresponding to initial state R_0

δ

To find:

All states reachable from R_0 in 1, 2, 3, ... clock ticks


Strategy: Denote set of states reachable from R_0 in k (or less) clock ticks as R_k

Express R_k as a function of R_{k-1} and δ and solve recurrence relation

- Remember: Every set is represented as a Boolean function (BDD)

28

What's the initial state?

 


29

Computing R_k , $k \geq 1$

How do we define R_{k+1} in terms of R_k and δ ?

(think in terms of sets)

- Is R_k inside R_{k+1} ?

 

30


Computing R_k , $k \geq 1$

Describing the edge in math notation:

$$s \in R_k$$

$$s^+ \in R_{k+1}$$

$$\delta(s, x, s^+) = 1$$

 

31

Looking at it another way...

Suppose I gave you a s^+ and asked you whether it was in R_{k+1} , i.e.: When is $R_{k+1}(s^+) = 1$? What are the cases?

Answer this question in terms of R_k and δ ?
(in English)

Either

1. s^+ is in R_k , i.e., $R_k(s^+) = 1$

Or

2.

There exist current state s and input x such that:

- $R_k(s) = 1$
- $\delta(s, x, s^+) = 1$

32

Writing out an equation for R_{k+1}

$$R_{k+1}(s^+) = R_k(s^+) + \exists s, x \{ R_k(s) \cdot \delta(s, x, s^+) \}$$

Either

1. s^+ is in R_k , i.e., $R_k(s^+) = 1$

Or

2.

There exist current state s and input x such that:

- $R_k(s) = 1$
- $\delta(s, x, s^+) = 1$

33

Computing R_k

Start with R_0

Repeatedly compute R_{k+1} as:

$$R_{k+1}(s^+) = R_k(s^+) + \exists s, x \{ R_k(s) \cdot \delta(s, x, s^+) \}$$

Note: everything is represented as a Boolean function


When do we stop?

34

Termination

When R_k and R_{k+1} are the same

Why is this guaranteed to happen?

 

35

Recap of Reachability Analysis

Compute start state R_0

Compute expression for δ

Repeatedly compute R_k until termination
criterion is true

Resulting R_k for largest k is the set of all states
reachable from R_0

36

Sequential Equivalence Checking

Connect the two FSMs to form combined FSM

Compute combined start state R_0

Compute expression for δ

Repeatedly compute R_k for increasing k until termination criterion is true

The R_k for largest k is the set of all states reachable from R_0

Check if any of these states can generate output 0 (showing that the two FSM outputs are different) → **HOW?**

37

Sequential Equivalence Checking

Connect the two FSMs to form combined FSM

Compute combined start state R_0

Compute expression for δ

Repeatedly compute R_k for increasing k until termination criterion is true

The R_k for largest k is the set of all states reachable from R_0

Check if any of these states can generate output 0 (showing that the two FSM outputs are different) → **Check if the Boolean function $R_k(s) \cdot \bar{z}(s)$ is satisfiable, satisfying assignment is the state in which outputs differ**

38

Summary

**Sequential equivalence checking can be done using
FSM reachability analysis**

In practice, very computationally intensive

- Memory intensive: BDDs can grow quite big

**Currently limited to a few hundred to few thousand
state bits**

Scaling this up is an active area of research

- New techniques based on SAT solving are available: e.g.,
the ABC system developed in Prof. Brayton's group at
Berkeley